

Experiment 6: Music Synthesizer

Rathour Param Jitendrakumar Roll Number: 190070049

EE-214, WEL, IIT Bombay

April 03, 2021

Overview of the experiment:

The purpose of this experiment is to design an automated music synthesizer using FSM and the seven major notes in the Indian classical music named sa, re, ga, ma, pa, dha, ni (lower octave) & Sa (upper octave). Describe it in VHDL using Behavioral Modelling, simulate with the given test-bench using Quartus.

I used the provided skeleton code, designed the circuit accordingly, verified my implementation using Register-transfer level simulation & observed the music by mapping it to the Krypton board interfaced with speaker.

This report contains my approach to the experiment, the circuit's design with the relevant code followed by the RTL netlist view, PIN planning and design confirmation by output waveforms of RTL.

Approach to the experiment:

Note	Sa	Ga	Sa	Ga	Sa	Ga	Ma	Ga	Re	Sa
Duration	0.5s	0.5s	0.5s	0.5s	0.5s	0.5s	0.25s	0.25s	0.25s	0.25s
Count	1,2	3,4	5,6	7,8	9,10	11,12	13	14	15	16


Note	Ni	Re	Ni	Re	Ni	Re	Ga	Re	Sa	Ni
Duration	0.5s	0.5s	0.5s	0.5s	0.5s	0.5s	0.25s	0.25s	0.25s	0.25s
Count	17,18	19,20	21,22	23,24	25,26	27,28	29	30	31	32

I used FSM based approach such that note will be played one after another in the given sequence. I generated a 4Hz Clock so that a note is played for a particular duration (in multiples of 0.25 seconds) as shown in table.

This FSM was realised using Behavioral approach (switch statement). With 5 distinct notes to be played and a silent state, we can make FSM with 6 states (Silent, Sa, Re, Ga, Ma, Ni). The corresponding State Transition Diagram and State Transition Table are shown.

Transitions occur at positive edge of 4Hz clock. In my approach, present state and present value of count is used to go to next state, and then I increment the value of count.


Press Reset to go back to Silent state

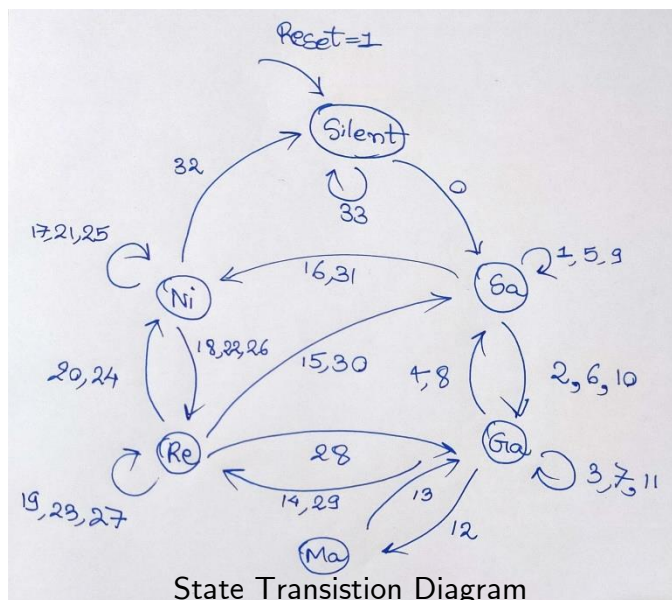

State Transition Table

Current State	Reset	Count	Next State
Silent	1	X	Silent
Silent	0	0	Sa
Silent	0	33	Silent
Sa	1	X	Silent
Sa	0	1	Sa
Sa	0	2	Ga
Sa	0	5	Sa
Sa	0	6	Ga
Sa	0	9	Sa
Sa	0	10	Ga
Sa	0	16	Ni
Sa	0	31	Ni
Re	1	X	Silent
Re	0	15	Sa
Re	0	19	Re
Re	0	20	Ni
Re	0	23	Re
Re	0	24	Ni
Re	0	27	Re
Re	0	28	Ga
Re	0	30	Sa

Current State	Reset	Count	Next State
Ga	1	X	Silent
Ga	0	3	Ga
Ga	0	4	Sa
Ga	0	7	Ga
Ga	0	8	Sa
Ga	0	11	Ga
Ga	0	12	Ma
Ga	0	14	Re
Ga	0	29	Re
Ma	1	X	Silent
Ma	0	13	Ga
Ni	1	X	Silent
Ni	0	17	Ni
Ni	0	18	Re
Ni	0	21	Ni
Ni	0	22	Re
Ni	0	25	Ni
Ni	0	26	Re
Ni	0	32	Silent
Pa	X	X	Silent
Dha	X	X	Silent

 

Tone Generation

Tone Generation approach as shown in flow chart.

To generate these frequencies, I used clock divider and onboard clock, calculated count for each note using

$$\text{Count} = 50 \text{ MHz} / (2 * f)$$

Note	Frequency (Hz)	Calculations (Truncated till 2 decimal places)		Count Value (Accurate to nearest integer)
Sa	240	$50 * 10^6 / (2 * 240)$	104166.66	104167
Re	270	$50 * 10^6 / (2 * 270)$	92592.59	92593
Ga	300	$50 * 10^6 / (2 * 300)$	83333.33	83333
Ma	320	$50 * 10^6 / (2 * 320)$	78125	78125
Pa	360	$50 * 10^6 / (2 * 360)$	69444.44	69444
Dha	400	$50 * 10^6 / (2 * 400)$	62500	62500
Ni	225	$50 * 10^6 / (2 * 225)$	111111.11	111111
Sa (upper octave)	480	$50 * 10^6 / (2 * 480)$	52083.33	52083
Clock_music	4	$50 * 10^6 / (2 * 4)$	6250000	62500000

Design document and VHDL code if relevant:

This whole design is part of music with 2 input bit & 9 output (with 8 LED bits to confirm our design).

See [music Input/Output Format](#)

I am using Behavioral Modelling for this experiment.

Modified toneGenerator entity from previous experiment is used.

Code can be broken down as shown in [approach](#)

Entity declaration

```
entity music is
port (toneOut : out std_logic;
      clk_50, resetn : in std_logic;
      LED : out std_logic_vector(7 downto 0));
end entity music;
```

Architechture of toneGenerator

```
architecture fsm of music is
-- Fill all the states
-- Declare state types here
type state_type is (Silent,sa,re,ga,ma,ni);
-- Declare all necessary signals here
signal y_present : state_type;
signal count : integer := 0;
signal noteInput : std_logic_vector(7 downto 0);
-- Take the toneGenerator component
component toneGenerator is
port (
switch : in std_logic_vector(7 downto 0);
clk : in std_logic;
LED : out std_logic_vector(7 downto 0);
toneOut : out std_logic);
-- This pin will give your notes output
end component toneGenerator;

begin

process(clk_50,resetn)
-- Fill sensitivity list
variable y_next_var : state_type;
variable n_count : integer := 0;
variable timecounter : integer range 0 to 1E8 := 1;
variable clock_music: std_logic := '0';

begin
y_next_var := y_present;
n_count := count;
```

Code for each state

```

case y_present is
  WHEN Silent => -- If the machine in Silent state
    if (resetn = '1') then
      y_next_var := Silent;
      noteInput <= "00000000";
    elsif (count = 0) then
      y_next_var := sa;
      noteInput <= "00000001";
      n_count := count + 1;
    elsif (count = 33) then
      y_next_var := Silent;
      noteInput <= "00000000";
    else
      y_next_var := y_present;
    end if;

```

```

WHEN sa => -- If the machine in Sa state
  if (resetn = '1') then
    y_next_var := Silent;
    noteInput <= "00000000";
  elsif ((count = 1) or (count = 5) or (count = 9)) then
    y_next_var := sa;
    noteInput <= "00000001";
    n_count := count + 1;
  elsif ((count = 2) or (count = 6) or (count = 10)) then
    y_next_var := ga;
    noteInput <= "00000100";
    n_count := count + 1;
  elsif ((count = 16) or (count = 31)) then
    y_next_var := ni;
    noteInput <= "01000000";
    n_count := count + 1;
  else
    y_next_var := y_present;
    noteInput <= "00000001";
  end if;

```

```

WHEN re => -- If the machine in Re state
  if (resetn = '1') then
    y_next_var := Silent;
    noteInput <= "00000000";
  elsif ((count = 19) or (count = 23) or (count = 27)) then
    y_next_var := re;
    noteInput <= "00000010";
    n_count := count + 1;
  elsif ((count = 15) or (count = 30)) then
    y_next_var := sa;
    noteInput <= "00000001";
    n_count := count + 1;
  elsif ((count = 20) or (count = 24)) then
    y_next_var := ni;
    noteInput <= "01000000";
    n_count := count + 1;
  elsif (count = 28) then
    y_next_var := ga;
    noteInput <= "00000100";
    n_count := count + 1;
  else
    y_next_var := y_present;
    noteInput <= "00000010";
  end if;

```

```

WHEN ga => -- If the machine in Ga state
  if (resetn = '1') then
    y_next_var := Silent;
    noteInput <= "00000000";
  elsif ((count = 3) or (count = 7) or (count = 11)) then
    y_next_var := ga;
    noteInput <= "00000100";
    n_count := count + 1;
  elsif ((count = 4) or (count = 8)) then
    y_next_var := sa;
    noteInput <= "00000001";
    n_count := count + 1;
  elsif ((count = 12)) then
    y_next_var := ma;
    noteInput <= "00001000";
    n_count := count + 1;
  elsif ((count = 14) or (count = 29)) then
    y_next_var := re;
    noteInput <= "00000010";
    n_count := count + 1;
  else
    y_next_var := y_present;
    noteInput <= "00000100";
  end if;

```

```

WHEN ma => -- If the machine in Ma state
  if (resetn = '1') then
    y_next_var := Silent;
    noteInput <= "00000000";
  elsif (count = 13) then
    y_next_var := ga;
    noteInput <= "00000100";
    n_count := count + 1;
  else
    y_next_var := y_present;
    noteInput <= "00001000";
  end if;

```

```

WHEN ni => -- If the machine in Ni state
  if (resetn = '1') then
    y_next_var := Silent;
    noteInput <= "00000000";
  elsif ((count = 17) or (count = 21) or (count = 25)) then
    y_next_var := ni;
    noteInput <= "01000000";
    n_count := count + 1;
  elsif ((count = 18) or (count = 22) or (count = 26)) then
    y_next_var := re;
    noteInput <= "00000010";
    n_count := count + 1;
  elsif (count = 32) then
    y_next_var := Silent;
    noteInput <= "00000000";
    n_count := count + 1;
  else
    y_next_var := y_present;
    noteInput <= "01000000";
  end if;

```

Else Condition

```

  WHEN others =>
    y_next_var := Silent;
    noteInput <= "00000000";
    n_count := 0;
END CASE ;

```


Clock generation and state transition


```
if (clk_50 = '1' and clk_50' event) then -- clk_50 is 0 to 1 (positive edge)
  if (resetn = '0') then
    if timecounter = 625000 then -- Generate 4Hz clock (0.25s time period) from 50MHz clock (clock_music)
      timecounter := 1; -- When it reaches max count i.e. 625000 (1/8 of a second) it will be 0 again
      if (clock_music = '1') then
        y_present <= y_next_var; -- State transition
        count <= n_count; -- Update count value
      end if;
      clock_music := not clock_music; -- This variable will toggle clock_music
    else
      timecounter := timecounter + 1; -- Counter will be incremented till it reaches max count
    end if;
  elsif (resetn = '1') then -- If reset is 1 then output should be 0
    timecounter := 1;
    clock_music := '0';
    y_present <= Silent;
    count <= 0;
  end if;
end if;
end process;
```

Instantiate toneGenerator component

```
comp: toneGenerator port map (switch => noteInput, clk => clk_50, LED => LED, toneOut => toneOut);
```

Netlist View:

 

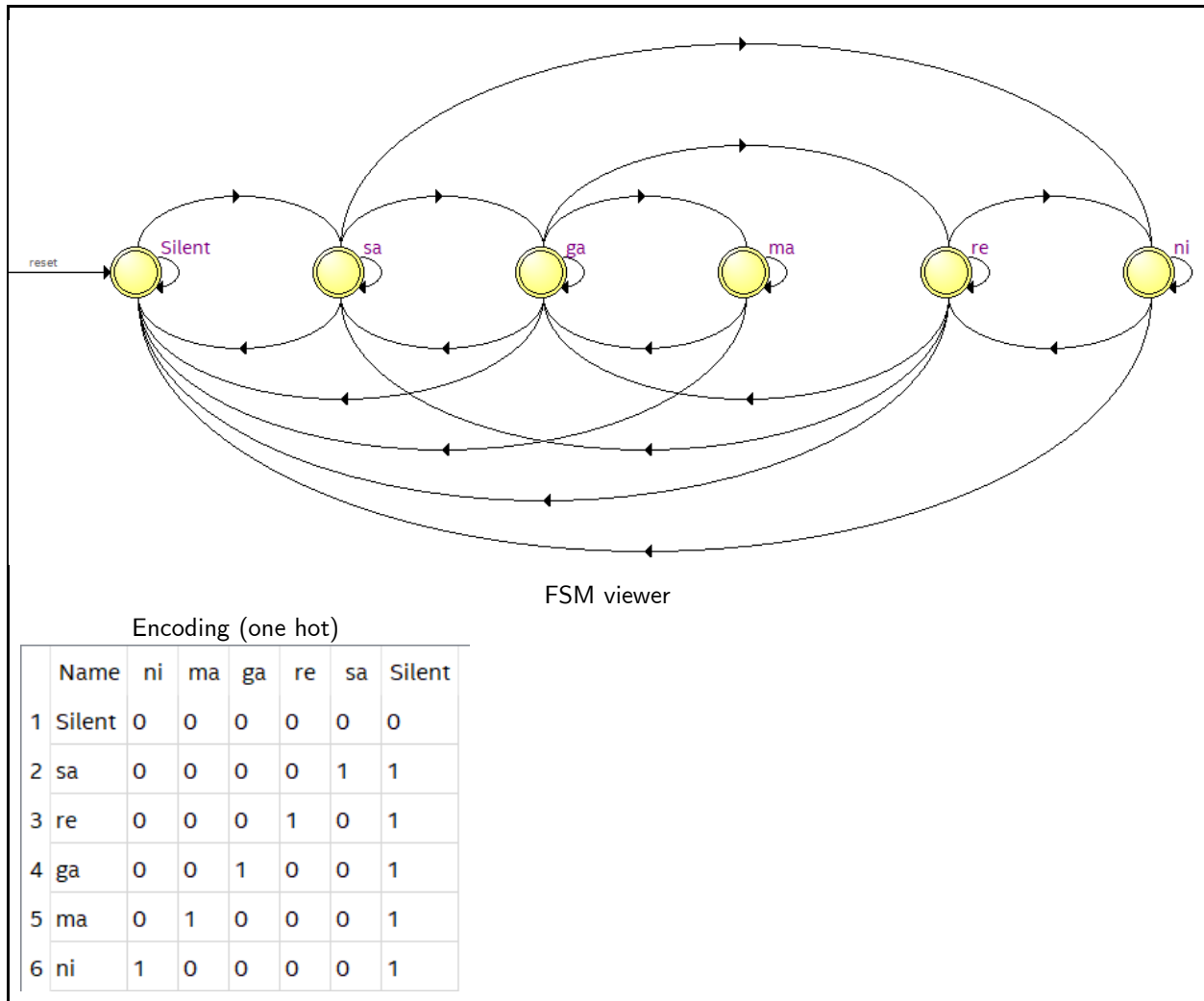

music Input/Output Format:

Input Format: CS	(C (Onboard Clock) & S (Reset Switch))
Output Format: OL ₈ L ₇ L ₆ L ₅ L ₄ L ₃ L ₂ L ₁	(O is output & 8-bit number L (L ₈ is MSB L ₁ is LSB))
Here, output to speaker oscillates between 0 and 1 according to frequencies of notes and L _i will glow (other LEDs are OFF) when corresponding note is played.	


RTL Simulation:




Gate-level Simulation:

Gate-level Simulation takes a lot of time and my computer crashes.

Krypton board:

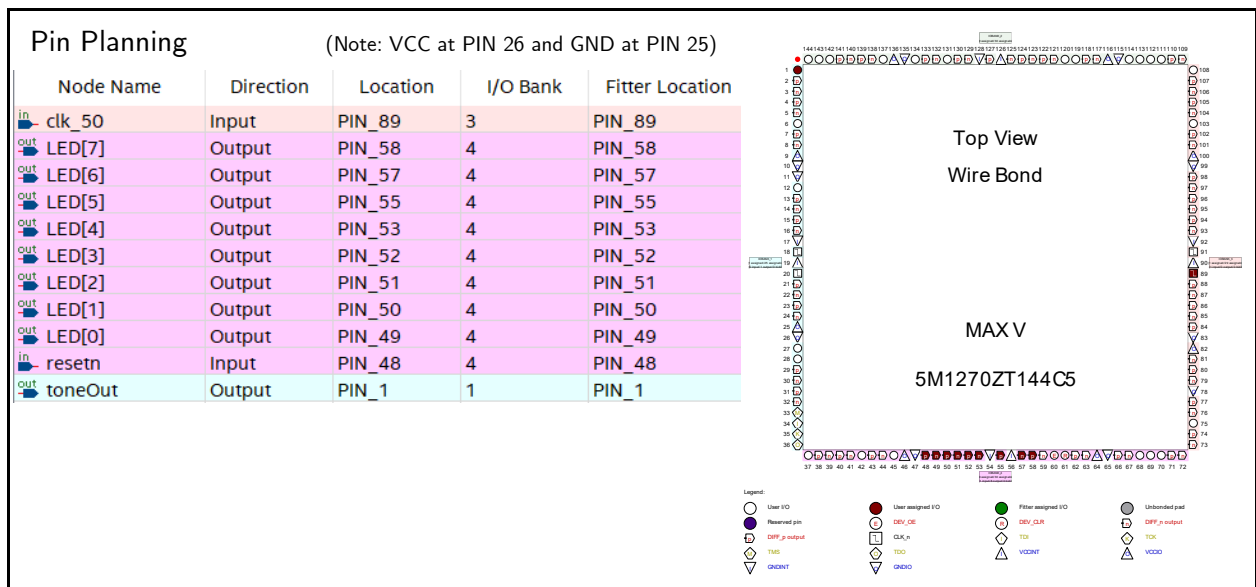

Board

 

Observations:

Observed frequencies from RTL simulation are very close to required frequencies

Music starts as soon as board is powered ON. By toggling reset switch (S1) music can be turned OFF when reset is ON and then turned ON again by swithing OFF reset pin.

References:

Tertulien Ndjountche *Digital Electronics 3 Finite State Machines Circuits* Wiley