



State transition diagram

$$Q = \{ \phi, s_a, s_b, s_{ab}, s_{ba}, s_{aba}, s_{bab} \}$$

$$\Sigma = \{ a, b, \text{reset} \}$$

$$\Lambda = \{ \gamma, N \}$$

$$\delta: \Sigma \times Q \rightarrow Q$$

$$\lambda: \Sigma \times Q \rightarrow \Lambda$$

Binary Encoding (compact encoding)

• For input

x_1	x_0	Symbol
0	0	a b
0	1	b a
1	0	reset
	1	don't care

• For output

y_0	Symbol
0	N
1	Y

• For State

q_2	q_1	q_0	Symbol
0	0	0	\emptyset
0	0	1	Sa
0	1	0	Sb
0	1	1	Sab
1	0	0	Sba
1	0	1	Saba
1	1	0	Sbab
1	1	1	---

When input is reset output is zero

Binary Encoding (One hot encoding)

• For input

x_1	x_0	Symbol
0	0	Reset
0	1	a
1	0	b

Not used later
in design

• For output

y_1	y_0	Symbol
0	1	N
1	0	Y

• For state

q_6	q_5	q_4	q_3	q_2	q_1	q_0
0	0	0	0	0	0	1
0	0	0	0	0	1	0
0	0	0	0	1	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
1	0	0	0	0	0	0

Symbol |

ϕ
 S_a

S_b

S_{ab}

S_{ba}

S_{aba}

S_{bab}

When input is reset output is zero

This can be done by taking \downarrow NOR with output
reset

So, where output depends on only x_2
Then final output = x_1 NOR output

Same thing can be done for state transition function

NOR output with x_1
 q_2, q_1, q_0

State functions & Output functions

Present state			Input	Next State			Output
q_2	q_1	q_0	x_0	q_2'	q_1'	q_0'	y_0
0	0	0	0	0	1	0	0
0	0	0	1	0	0	1	0
0	0	1	0	0	1	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	1	0	0	0
0	1	1	0	0	1	0	0
0	1	1	1	1	0	1	0
1	0	0	0	1	1	0	0
1	0	0	1	0	0	1	0
1	0	1	0	1	1	0	1
1	0	1	1	0	0	1	0
1	1	0	0	0	1	0	1
1	1	0	1	1	0	1	1

δ for q_2

$q_2 \backslash q_1$	00	01	11	10
00	0_0	0_1	0_3	0_2
01	0_4	0_5	0_7	0_6
11	0_{12}	0_{13}	X_{15}	X_{14}
10	0_8	0_9	0_{11}	0_{10}

Squad
+ Pair

$$\delta q_2 = q_1 x_0 + q_2 \bar{q}_1 \bar{x}_0$$

δ for q_1

$q_2 \backslash q_1$	00	01	11	10
00	1_0	0_1	0_3	1_2
01	1_4	0_5	0_7	1_6
11	1_{12}	0_{13}	X_{15}	X_{14}
10	1_8	0_9	0_{11}	1_{10}

Octet

$$\delta q_1 = \bar{x}_0$$

δ for q_0

$q_2 \backslash q_1$	00	01	11	10
00	0_0	1_1	1_3	1_2
01	0_4	0_5	1_7	0_6
11	0_{12}	1_{13}	X_{15}	X_{14}
10	0_8	1_9	1_{11}	0_{10}

2 Squad
2 Pair

$$\delta q_0 = q_2 x_0 + q_0 x_0 + \bar{q}_2 \bar{q}_1 x_0 + \bar{q}_2 \bar{q}_1 q_0$$

for output y

$q_2 q_1$ \ q_0	00	01	11	10
00	0 ₀	0 ₁	0 ₃	0 ₂
01	0 ₄	0 ₅	0 ₇	0 ₆
11	0 ₁₂	1 ₁₃	X ₁₅	X ₁₄
10	0 ₈	0 ₉	0 ₁₁	1 ₁₀

2 pairs

$$\lambda = q_2 q_1 q_0 + q_2 q_1 \overline{q_0}$$

to accommodate reset

$$\lambda_{\text{final}} = x_1 \text{ NOR } (\lambda)$$

$$\delta_{\text{final}} = \sum x_1 \text{ NOR } \sum_{\substack{q_2 q_1 q_0 \\ \text{provided}}} \delta$$

for each q_2, q_1, q_0

To implement AND we can do NAND then NOT
 To implement OR we can do NOR then NOT

Final design

